

Basic wiring for a LED trailer on a Land Rover Disco 3 or 4


This can be used to overcome the "pulsing" found with LED lights on a Discovery 3 (or similar). You can choose to make your own transferable box to mount it in or wire it straight into the trailer.

The LR12 Load resistor is approx \$15 each, the Relay is around \$10 each

Trailer wiring colours

- 1 tail, clearance - **brown**
- 2 left hand turn - **yellow**
- 3 right hand turn - **green**
- 4 stop - **red**
- 5 electric brakes - **blue**
- 6 earth - **white**

12V SPDT Relay (Bosch or other)

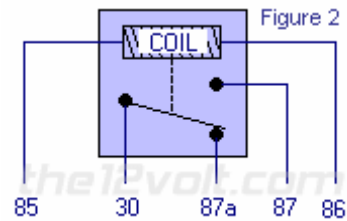

LR12 Load Resistor (available from most trailer or auto electrical specialist)

